

Problem	Points	Score
1	10	
2	10	
3	15	
4	15	
5	15	
6	20	
7	15	
Total	100	

```

ENTITY __entity_name IS
    PORT(__input_name, __input_name      : IN STD_LOGIC;
         __input_vector_name           : IN STD_LOGIC_VECTOR(__high downto __low);
         __bidir_name, __bidir_name     : INOUT STD_LOGIC;
         __output_name, __output_name   : OUT STD_LOGIC);
END __entity_name;

```

```

ARCHITECTURE a OF __entity_name IS
    SIGNAL __signal_name : STD_LOGIC;
    SIGNAL __signal_name : STD_LOGIC;
BEGIN
    -- Process Statement
    -- Concurrent Signal Assignment
    -- Conditional Signal Assignment
    -- Selected Signal Assignment
    -- Component Instantiation Statement
END a;

```

```

SIGNAL __signal_name : __type_name;
__instance_name: __component_name GENERIC MAP (__component_par => __connect_par)
PORT MAP (__component_port => __connect_port,
           __component_port => __connect_port);

```

```

WITH __expression SELECT
    __signal <= __expression WHEN __constant_value,
    __expression WHEN __constant_value,
    __expression WHEN __constant_value,
    __expression WHEN __constant_value;

```

SELECT assignment statement

```

__signal <= __expression WHEN __boolean_expression ELSE
    __expression WHEN __boolean_expression ELSE
    __expression;

```

Conditional assignment statement

```

IF __expression THEN
    __statement;
    __statement;
ELSIF __expression THEN
    __statement;
    __statement;
ELSE
    __statement;
    __statement;
END IF;

```

```

<optional_label>:
    FOR <loop_id> IN <range> LOOP
        -- Sequential Statement(s)
    END LOOP;

```

```

WAIT UNTIL __expression;

```

```

CASE __expression IS
    WHEN __constant_value =>
        __statement;
        __statement;
    WHEN __constant_value =>
        __statement;
        __statement;
    WHEN OTHERS =>
        __statement;
        __statement;
END CASE;

```

```

<generate_label>:
    FOR <loop_id> IN <range> GENERATE
        -- Concurrent Statement(s)
    END GENERATE;

```

1) (10 points) Fill in the waveform for the signals “result_add” and “result_sub” in decimal values

```

entity ALU is
  port (
    clk, rst : in std_logic;
    input1 : in std_logic_vector(7 downto 0);
    input2 : in std_logic_vector(7 downto 0);
    result_add, result_sub : out std_logic_vector(7 downto 0);
    overflow_add : out std_logic
  );
end ALU;

architecture BHV of ALU is
  signal temp_Add: std_logic_vector(8 downto 0);
begin
  process(clk, rst)
    variable temp_sub: std_logic_vector(8 downto 0);
  begin
    if(rst = '1') then
      result_add <= "00000000";
      result_sub <= "00000000";
      overflow_add <= '0';
    elsif (clk='1' and clk'event) then
      temp_Add <= std_logic_vector(unsigned("0" & input1) +
        unsigned("0" & input2));
      temp_sub:= std_logic_vector(unsigned("0" & input1) -
        unsigned("0" & input2));
      result_add <= temp_Add(7 downto 0);
      result_sub <= temp_sub(7 downto 0);
      overflow_add <= temp_Add(8);
    end if;
  end process;
end BHV;

```

Input1					
150	200	81	30	110	
Input2					
100	57	48	20	40	
Result_add					
X	X	250	1 (overflow)	129	50
Result_sub					
X	50	143	33	10	70

b) Explain the behavior of “result_add’s” value, mentioning when signals get updated.
 Signals are updated at the end of process, variables are updated immediately.
 Since temp_Add is defined as a signal, we need two cycles to see the correct value of Result_add.

2) (10 points) Identify violations (if any) of the synthesis guidelines for synthesizable logic and the effect on the synthesized circuit.

```
entity test is
port(
  input   : in std_logic_vector(3 downto 0);
  clk, rst : in std_logic;
  output  : out std_logic_vector(3 downto 0));
end test;

architecture BHV of test is
begin
process (clk, rst)
begin
  if (rst = '1') then
    output <= "0000";
  elsif (clk'event and clk = '1') then
    output <= std_logic_vector(unsigned(input)+ 1)
  end if;
end process;

process (input)
begin
  output <= std_logic_vector(unsigned(input) + 5);
end process;

end BHV;
```

Wait/time is not synthesizable!

after 10ns;

Output is derived in multiple processes
→ Multiple drivers for a signal

3) (15 points) A 16x1 multiplexer is provided as reference. Fill in the code for designing this module using structural descriptions of 4x1 multiplexers and generate statement.

```
entity mux4to1 is
port (w0, w1, w2, w3: in std_logic;
s : in std_logic_vector(1 downto 0) ;
f : out std_logic) ;
end mux4to1;
```

```
architecture BHV of mux4to1 is
begin
with s select
f <= w0 when "00",
w1 when "01",
w2 when "10",
w3 when others;
end BHV;
```


```
entity mux16to1 is
port (w : in std_logic_vector(0 downto 15);
s : in std_logic_vector(3 downto 0);
f : out std_logic);
end mux16to1;
```

```
architecture STR of mux16to1 is
component mux4to1
port (w0, w1, w2, w3: in std_logic;
s : in std_logic_vector(1 downto 0);
f : out std_logic );
end component;

signal m: std_logic_vector(3 downto 0);
begin
--code to be inserted
MuxGEN: for i in 0 to 3 generate
Muxes: mux4to1 port map
(w0=>w(4*i), w1=>w(4*i+1), w2=>w(4*i+2), w3=>w(4*i+3),
s=>s(1 DOWNTO 0), f=>m(i) ) ;
END GENERATE ;

--code to be inserted
Mux_last: mux4to1 port map
(w0=>m(0), w1=>m(1), w2=>m(2), w3=>m(3), s=>s(3 DOWNTO 2),
f=>f ) ;

end STR;
```

 

4) (8 points) (a) Define each carry bit of a 4-bit carry lookahead adder ($c(1)$, $c(2)$, $c(3)$, $c(4)$) in terms of the *propagate* and *generate* functions, and carry in ($c(0)$).

$$c(1) = g_0 + p_0 c(0)$$

$$c(2) = g_1 + p_1 c(1) = g_1 + p_1 g_0 + p_1 p_0 c(0)$$


$$c(3) = g_2 + p_2 c(2) = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c(0)$$

$$c(4) = g_3 + p_3 c(3) = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c(0)$$

(b) (2 points) Circle the Delay vs width graph that seems appropriate for carry lookahead adder (CLA):




 (c) (2 points) Circle the Area (# of gates) vs width graph that seems appropriate for carry lookahead adder (CLA):



(d) (3 points) True/false. A hierarchical carry-lookahead adder reduces area overhead compared to a single-level carry-lookahead adder without increasing propagation delay. **False**

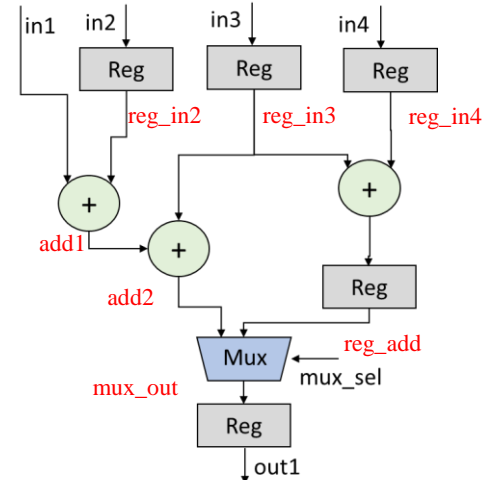5) (15 points) Fill in the following behavioral VHDL to implement the illustrated circuit. Assume that clk and rst connect to every register. All wires and operations are width bits. Ignore overflow from the adders.



```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
```

```
entity test1 is
generic (width : positive := 8);
port (
  clk, rst, mux_sel : in std_logic;
  in1, in2, in3, in 4 : in std_logic_vector(width-1 downto 0);
  out1: out std_logic_vector(width-1 downto 0));
end test1;
```

```
architecture BHV of test1 is
signal reg_in2, reg_in3, reg_in4, add1, add2, add3, reg_add, mux_out:
std_logic_vector(width-1 downto 0);
```

```
begin
process(clk, rst)
```

```
begin
if (rst = '1') then
  reg_in2 <= (others => '0');
  reg_in3 <= (others => '0');
  reg_in4 <= (others => '0');
  reg_add <= (others => '0');
  out1 <= (others => '0');
elsif (rising_edge(clk))

  reg_in2 <= in2;
  reg_in3 <= in3;
  reg_in4 <= in4;
  reg_add <= std_logic_vector(unsigned(reg_in3)+unsigned(reg_in4));

  if mux_sel = '0' then
    out1 <= add1;
  else
    out1 <= reg_add;
  end if;
```

```
end if;
end process;
add1 <= std_logic_vector(unsigned(in1) + unsigned(reg_in2));
add2 <= std_logic_vector(unsigned(add1) + unsigned(reg_in3));
```

```
end BHV;
```


6) (20 points) Given the following entity definition for a generic adder, Modify the testbench on the next page to:

- (a) To test the “adder” entity as a **32-bit** adder.
- (b) Make the testbench code general; i.e., can be used to test for any number of bits by changing only the value of **NBITS**.

You need to make all necessary changes to make it work with the generic adder from the previous page (**put changes right on the next page**)

```
entity adder is
    generic (WIDTH : positive := 8);
    port map (input1, input2 : in std_logic_vector (WIDTH-1 downto 0);
              carry_in : in std_logic;
              sum: out std_logic_vector (WIDTH-1 downto 0);
              carry_out: out std_logic);
end adder;
```

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity adder_tb is
end adder_tb;

architecture TB of adder_tb is
constant NBITS : positive := 16;
signal input1,input2,sum : std_logic_vector(NBITS-1 downto 0);
signal carry_in, carry_out : std_logic;
begin -- TB

UUT : entity work.adder
    port map (
        input1    => A-input1,
        input2    => B input2,
        carry_in  => C carry_in,
        sum       => D sum,
        carry_out => E carry_out);

process

-- function definitions here

begin
    for i in 0 to 15 2**NBITS-1 loop
        for j in 0 to 15 2**NBITS-1 loop
            for k in 0 to 1 loop
                input1  <= std_logic_vector(to_unsigned(i, 4 NBITS))
                input2  <= std_logic_vector(to_unsigned(j, 4 NBITS))
                carry_in <= std_logic(to_unsigned(k, 1)(0));
                wait for 40 ns;
                assert(sum = sum_test(i,j,k)) report "Sum incorrect";
                assert(carry_out = carry_test(i,j,k)) report "Carry incorrect";
            end loop; -- k
        end loop; -- j
    end loop; -- i
    report "SIMULATION FINISHED!";
    wait;
end process;
end TB;

```

```

function X carry_test (
    constant a, b, c:
integer)
return std_logic is
begin
    if (a + b + c > 15) then
        return '1';
    else return '0';
    end if;
end X carry_test;

function Y (
    constant a, b, c:
integer)
return std_logic is
begin
    return
std_logic_vector(to_unsigned(
        (a+b+c) mod
16, 4));
end Y;

function Z sum_test (
    constant a, b, c:
integer)
return std_logic_vector
is
begin
    return
std_logic_vector(to_unsigned(
        (a+b+c) mod
16-2**NBITS, 4- NBITS));
end Z sum_test;

```

7) (15 points) Fill in the skeleton code to implement the following Moore finite state machine, using the 2-process FSM model. Assume that if an edge does not have a corresponding condition, that edges always taken on a rising clock edge. Assume that INIT is the start state. Use the next page if extra room is needed.


```
library ieee;
use ieee.std_logic_1164.all;
entity fsm is
port (
clk, rst, go, Done : in std_logic;
X : out std_logic_vector(1 downto 0));
end fsm;
```

```
architecture PROC2 of fsm is
type STATE_TYPE is (INIT, COUNT1, COUNT2, DONE, GO);
signal state, next_state : STATE_TYPE;
begin
process(clk, rst)
begin
if (rst = '1') then
Stata <= INIT;

elseif (clk'event and clk = '1') then

State <= next_state;
end if;
end process;
```
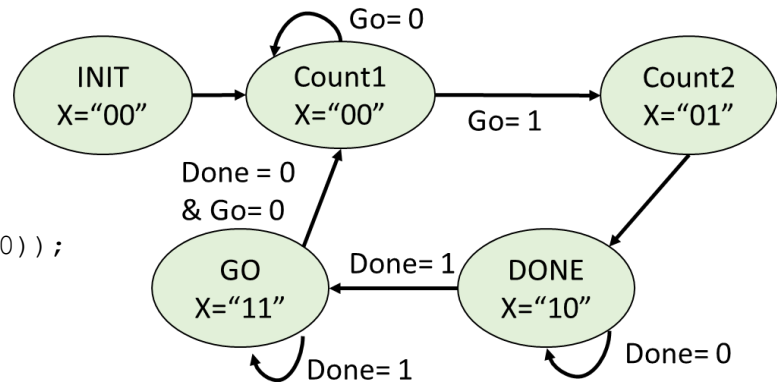
```
process ( go, done, state)
begin
next_state <= state;
X <= "00";
Case state is
When INIT =>
Next_state <= COUNT1;
X <= "00";
When COUNT1 =>
If go = '1' then
Next_state <= COUNT2;
End if;
X <= "00";
When COUNT2 =>
Next_state <= DONE;
X <= "01";
When DONE =>
If done = '1' then
Next_state <= GO;
End if;
X <= "10";
```



```
When GO =>
    If done = '0' and go = '0' then
        Next_state <= COUNT1;
    End if;
    X <= "11";
When others => null;
End case;
```

```
end process;
end PROC2;
```